

COS10004 – Computer Systems

Name: Nguyen Manh Dung

Student ID: SWH01226


2.1. List the major components you believe you will need to build to achieve this?

- In order to build the circuit I will need parts like registers, flip-flops, gates, cables, and hex displays to make it.

2.2. What resources (lecture slides, previous labs, online links etc) do you have that are relevant to these components ?

- I'm utilizing my lab work, old lecture slides, and websites like <https://www.electronics-tutorials.ws/> to help me with my job.

3.

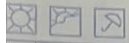

Mo Tu We Th Fr Sa Su

Memo No. _____

Date / /

Assignment 1

